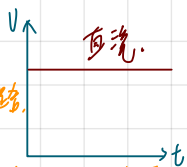


1. (10) Compare DC power system with AC power system.

直流電力系統

①: 電感短路, 電容開路,
∴ 沒有虛功.

② 傳統的無源升壓降壓轉換: 近代靠電力電子





交流電力系統


① 介: 單相及三相

② 電感、電容不能忽略。
∴ 產生虛功。

③ 利用變壓器升壓 ∴ 減少傳輸線損失再降壓提供負載使用。

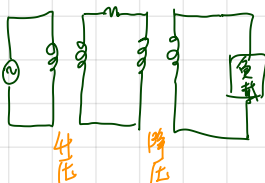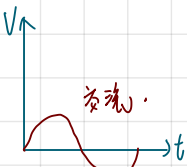


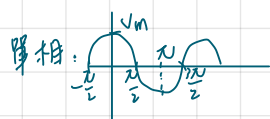2. (10) Compare AC single phase voltage with three phase voltage.



$$v(t) = V_m \cdot \sin \omega t$$

缺點: Power 脈動。
電力是抖動的

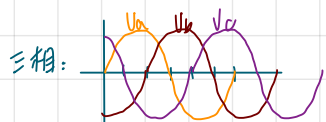

優點: Power 是常數 = $3 \cdot V_{\text{相}} \cdot I_{\text{相}} \cos \theta = \sqrt{3} V_{\text{line-to-line}} \cdot I_{\text{line-to-line}} \cos \theta$
(線對線)

$$v_a(t) = V_m \cdot \sin \omega t$$

$$v_b(t) = V_m \cdot \sin(\omega t - 120^\circ) = V_m \sin(\omega t - \frac{2}{3}\pi)$$

$$v_c(t) = V_m \cdot \sin(\omega t - 240^\circ)$$


3. (10) A generator will be paralleled with a running AC power system. Which conditions are required for paralleling?

併網條件: ① 頻率 (f 頻率, $\omega = 2\pi f$ 角速度) 一樣。
② 角度一樣
③ 相序一樣
④ V_m (振幅) 一樣。

4. (10) Plotting the generator phasor diagrams under (a) lagging power factor; (b) unity power factor; (c) leading power factor.


相量圖在同步座標。

(a) 落後功因, (b) 單位功因, (c) 領先功因。

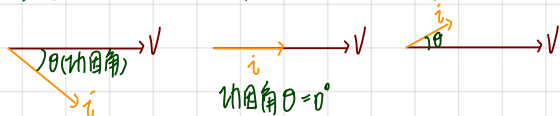

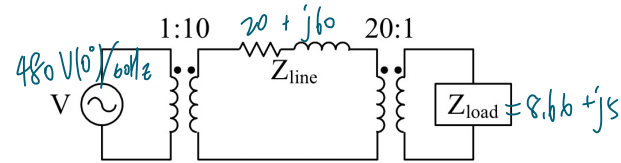5.(20) A simple power system is shown in figure. This system contains a 480V(0°)/60Hz generator connected to an ideal 1:10 step-up transformer, a transmission line, an ideal 20:1 step-down transformer, and a load. The impedance of the transmission line is $Z_{\text{line}} = 20 + j60 \Omega$, and $Z_{\text{load}} = 8.66 + j5 \Omega$. The base values for this system are chosen to be 480V and 10kVA at the generator.

- Find the base voltage, current, impedance, and apparent power at every point in the power system.
- Convert this system to its per-unit equivalent circuit.
- Find the power supplied to the load in this system.
- Find the power lost in the transmission line



(a) I. In the generator region:

$$\begin{aligned} V_{\text{base}1} &= 480 \text{ V}; \quad S_{\text{base}} = 10 \text{ kVA} = 10000 \text{ VA} \\ I_{\text{base}1} &= \frac{S_{\text{base}}}{V_{\text{base}1}} = \frac{10000 \text{ VA}}{480 \text{ V}} = 20.83 \text{ A} \\ Z_{\text{base}1} &= \frac{V_{\text{base}1}}{I_{\text{base}1}} = \frac{480 \text{ V}}{20.83 \text{ A}} = 23.04 \Omega \end{aligned}$$

II. In the transmission line region:

$$\begin{aligned} V_{\text{base}2} &= 10 \cdot V_{\text{base}1} = 10 \times 480 = 4800 \text{ V}; \quad S_{\text{base}} = 10000 \text{ VA} \\ I_{\text{base}2} &= \frac{S_{\text{base}}}{V_{\text{base}2}} = \frac{10000 \text{ VA}}{4800 \text{ V}} = 2.083 \text{ A} \\ Z_{\text{base}2} &= \frac{V_{\text{base}2}}{I_{\text{base}2}} = \frac{4800 \text{ V}}{2.083 \text{ A}} = 2304 \Omega \end{aligned}$$

III. In the load region:

$$\begin{aligned} V_{\text{base}3} &= \frac{1}{20} V_{\text{base}2} = \frac{1}{20} \times 4800 = 240 \text{ V}; \quad S_{\text{base}} = 10000 \text{ VA} \\ I_{\text{base}3} &= \frac{S_{\text{base}}}{V_{\text{base}3}} = \frac{10000 \text{ VA}}{240 \text{ V}} = 41.67 \text{ A} \\ Z_{\text{base}3} &= \frac{V_{\text{base}3}}{I_{\text{base}3}} = \frac{240 \text{ V}}{41.67 \text{ A}} = 5.76 \Omega \end{aligned}$$

(b) I. In the generator region:

$$V_{\text{G,pu}} = \frac{V_{\text{G}}}{V_{\text{base}1}} = \frac{480 \angle 0^\circ \text{ V}}{480 \text{ V}} = 1.0 \angle 0^\circ \text{ pu}$$

II. In the transmission line region:

$$Z_{\text{line,pu}} = \frac{Z_{\text{line}}}{Z_{\text{base}2}} = \frac{20 + j60 \Omega}{2304 \Omega} = 0.0087 + j0.026 \text{ pu}$$

III. In the load region:

$$Z_{\text{load,pu}} = \frac{Z_{\text{load}}}{Z_{\text{base}3}} = \frac{8.66 + j5 \Omega}{5.76 \Omega} = 1.503 + j0.868 \text{ pu}$$

$$(c) I_{\text{pu}} = \frac{V_{\text{pu}}}{Z_{\text{tot,pu}}} = \frac{1 \angle 0^\circ}{0.0087 + j0.026 + 1.503 + j0.868 \text{ pu}} = 0.4901 - j0.2898 \text{ pu} = 0.569 \angle -30.6^\circ \text{ pu}$$

$$P_{\text{load,pu}} = I_{\text{pu}}^2 \cdot P_{\text{load,pu}} = (0.569)^2 \cdot 1.503 = 0.489$$


$$P_{\text{load}} = P_{\text{load,pu}} \cdot S_{\text{base}} = 0.489 \times 10000 \text{ VA} = 4890 \text{ W}$$

$$(d) P_{\text{line,pu}} = I_{\text{pu}}^2 R_{\text{line,pu}} = (0.569)^2 (0.0087) = 0.00282$$

$$P_{\text{line}} = P_{\text{line,pu}} S_{\text{base}} = 0.00282 \times 10000 \text{ VA} = 28.2 \text{ W}$$


shift + 2, diff 3.
↓

6.(20) $S_{G1}: V_1=1 \angle 0^\circ, S_{D1}=1, jQ_{G2}: V_2=? \rightarrow S_{D2}=1, Z=j0.5$, (a) Find Q_{G2} for $|V_2|=1$ (b) and $\angle V_2$? (c) If $Q_{G2}=0$, could be supplied load S_{D2} ? (d) and $\angle V_2$?

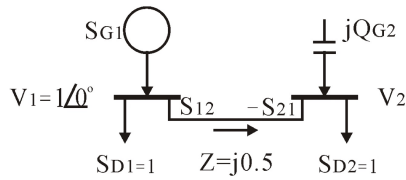

$$S = P + jQ$$

$$\begin{cases} P_{12} = -P_{21} = \frac{|V_1||V_2|}{X} \sin \theta_{12} \\ Q_{12} = \frac{|V_1|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12} \\ Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12} \end{cases}$$

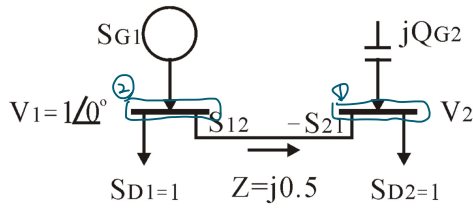

$$\textcircled{1} jQ_{G2} - S_{21} = 1 \Rightarrow \frac{P_{21}}{S_{P_{12}}=1} ; Q_{21} = Q_{G2}$$

$$\textcircled{2} S_{G1} = 1 + S_{12}$$

$$\Rightarrow S_{12} = -1$$

$$\textcircled{1} \textcircled{2} Q_{G2} = 0, \text{ find } S_{D2} \text{ \& } \angle V_2$$

Method I.

$$Q_{G2} = 0 \Rightarrow Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12} = 0$$

$$\Rightarrow |V_2| = |V_1| \cos \theta_{12}$$

$$\Rightarrow |V_2| = \cos \theta_{12} \Rightarrow \theta_{12} = 0$$


$$P_{12} = \frac{|V_1||V_2|}{X} \sin \theta_{12} = 1$$

$$\Rightarrow |V_2| \sin \theta_{12} = \frac{1}{2} \textcircled{2}$$

Method II.

$$\textcircled{1} \textcircled{2}: C_2 = -\frac{|V_2|^2}{|Z|} e^{j\angle Z} = -2|V_2|^2 j$$

$$\text{Magnitude: } |B| = \frac{|V_1||V_2|}{|Z|} = 2|V_2|$$

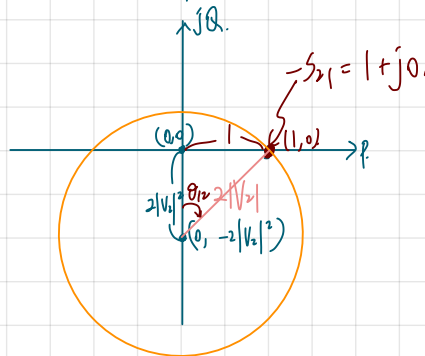

$$1^2 + (2|V_2|^2)^2 = 4|V_2|^2$$

$$4(|V_2|^2)^2 - 4|V_2|^2 + 1 = 0$$

$$\Rightarrow |V_2|^2 = \frac{1}{2} \Rightarrow |V_2| = \frac{1}{\sqrt{2}}$$

$$\Rightarrow \theta_{12} = 45^\circ \Rightarrow \angle V_2 = -45^\circ$$

(a) (b) $|V_2|=1$. Find $Q_{G2}, \angle V_2$

$$P_{12} = \frac{|V_1||V_2|}{X} \sin \theta_{12} = 1$$

$$\Rightarrow \frac{1 \times 1}{0.5} \sin \theta_{12} = 1$$

$$\Rightarrow \sin \theta_{12} = \frac{1}{2} \Rightarrow \theta_{12} = 30^\circ$$

$$\Rightarrow \theta_{12} = \theta_1 - \theta_2 = 30^\circ$$

$$\theta_2 = \theta_1 - 30^\circ = -30^\circ \therefore \angle V_2 = -30^\circ \#$$


$$Q_{G2} = Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12}$$

$$= \frac{1}{0.5} - \frac{1}{0.5} \cos 30^\circ$$

$$= 2 - 2 \cos 30^\circ = 0.2679 \#$$

7. (20) Find (a) S_{12} and S_{21} ; (b) P_{12} and $-P_{21}$; (c) Q_{12} and Q_{21} .

($Z=R+j\omega L$, $V_1=|V_1|e^{j\theta_1}$, $V_2=|V_2|e^{j\theta_2}$, $Z=|Z|e^{j\angle Z}$, $\theta_{12}=\theta_1-\theta_2$)

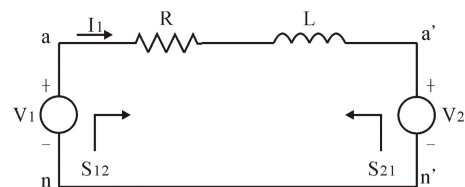

功率圓(短程) Complex power Circle

短程輸電線，用串聯的RL電路來表示電線 $Z=R+j\omega L$

$$(2.25) V_1=|V_1|e^{j\theta_1}, V_2=|V_2|e^{j\theta_2}, Z=|Z|e^{j\angle Z}, \theta_{12}=\theta_1-\theta_2$$

$$(2.26) S_{12}=V_1 I_1^*=V_1[(V_1-V_2)/Z]^*=|V_1|^2/(Z)^*-V_1 V_2^*/(Z)^* \\ =|V_1|^2 e^{j\angle Z}/|Z|-|V_1||V_2| e^{j\angle Z}e^{j\theta_{12}}/|Z|$$

$$(2.27) S_{21}=|V_2|^2 e^{j\angle Z}/|Z|-|V_1||V_2| e^{j\angle Z}e^{-j\theta_{12}}/|Z|$$

$$(2.28) -S_{21}=-|V_2|^2 e^{j\angle Z}/|Z|+|V_1||V_2| e^{j\angle Z}e^{-j\theta_{12}}/|Z|$$

$$(2.29) S_{12}=C_1-B e^{j\theta_{12}}, \quad \text{兩圓半徑均為 } |B|$$

$$(2.30) -S_{21}=C_2+B e^{-j\theta_{12}},$$

$$C_1=|V_1|^2 e^{j\angle Z}/|Z|, C_2=-|V_2|^2 e^{j\angle Z}/|Z|,$$

$$B=|V_1||V_2| e^{j\angle Z}/|Z|,$$

Assume $R=0$, $Z=jX \Rightarrow \angle Z=90^\circ$, $e^{j\angle Z}=j$

$$\text{So } (2.31) P_{12}=-P_{21}=(|V_1||V_2|/X)\sin\theta_{12}$$

$$(2.32) Q_{12}=|V_1|^2/X - (|V_1||V_2|/X)\cos\theta_{12}$$

$$(2.33) Q_{21}=|V_2|^2/X - (|V_1||V_2|/X)\cos\theta_{12}$$

