

# Power System Analysis

## 供電=用電

Arthur R. Bergen

授課：侯中權 博士

(Prof. Chung-Chuan Hou)



## 2.基本原理(Basic Principles)

2.0簡介(Introduction)

2.1供應單埠的複數功率(Complex Power Supplied to a One-Port)

2.2複數功率守恆(Conservation of Complex Power)

2.3平衡三相(Balanced Three-Phase)

2.4單相分析(Per Phase Analysis)

2.5平衡三相功率(Balanced Three-Phase Power)

2.6複數功率傳輸(短程)(Complex Power Transmission)

2.7複數功率傳輸(輻射線路) (Complex Power Transmission: Radial Line)

2.8結論與習題(Summary)

## 2.0簡介(Introduction)

1 直流電:被動元件(R,L,C);  $V=IR$ ,  $V=Ldi/dt$ ,  $I=Cdv/dt$

功率  $P=VI=V^2/R=I^2R$ ; 功  $J=P*t$

2 Kirchhoff's current law (KCL): sum of currents entering a node (or a closed boundary) is zero.

3 Kirchhoff's voltage law (KVL): sum of all voltages around a closed path (or loop) is zero.

4 穩態、暫態、動態 (steady state, transient state, dynamic state)



5 交流電:單相與三相;相量(phasor)

6 交流電:被動元件(R,L,C);  $v=iR$ ,  $v=Ldi/dt$ ,  $i=Cdv/dt$

功率  $P=V_{rms}I_{rms}=V_{rms}^2/R=I_{rms}^2R$ ; 功  $J=P*t$

7 符號:  $v_{BE}$ (總瞬間值) =  $V_{BE}$ (直流值) +  $v_{be}$ (交流瞬間值)


$V_{be}$ (相量值)

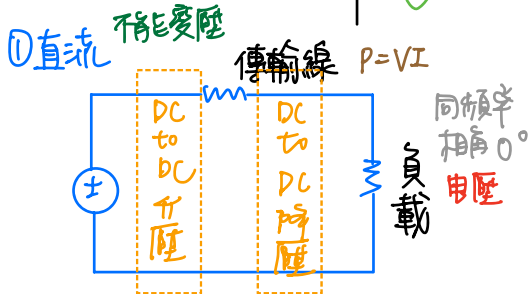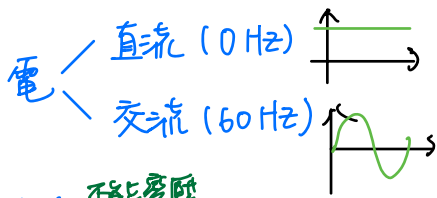

① 直流電：電壓，電流，(實)功率 (有儲能元件)

$$\begin{cases} V=IR \\ V=\frac{1}{C}\frac{di}{dt} \approx 0 \\ i=C\frac{dV}{dt} \approx 0 \end{cases} \quad P=VI=\frac{V^2}{R}=I^2R$$


② 交流 (RLC 都可當負載)

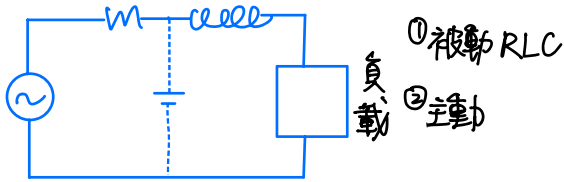


② 交流電：電壓，電流

視在功率 = 實功率 + 虛功率  
(R) (LC)
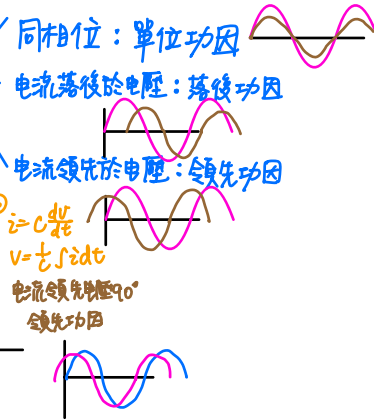
$$\begin{aligned} V &= IR & V &= \frac{1}{C}\frac{di}{dt} \\ \text{單位功因} & & \text{電流落後電壓 } 90^\circ & \\ \frac{d\sin t}{dt} &= \cos t = \sin(t+90^\circ) & \text{落後功因} & \end{aligned}$$



變壓器 (100 級發電機 + 許多) > 100 級變壓器 負載

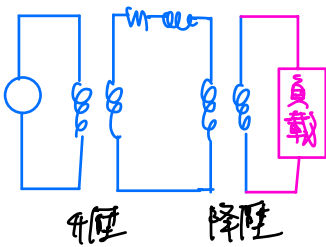

同頻率 = 所有發電機轉一樣快  
相角，電壓

電的 3 態

穩態 =  $t \rightarrow \infty$ , 留下的

暫態 =  $t \rightarrow \infty$ , 消失不見

瞬態 = 

$$y'' + 3y' + 2y = 5u(t)$$

輸入  $u(t)$ ,  $y(t)$  輸出

二階常微分方程式 非齊次

微分方程

特解: 通解  $y'' + 3y' + 2y = 0$  偏微分方程 (2個變數)

暫態解  $(D+3)(D+2)y=0$

穩態解  $(D+1)(D+2)y=0$

特解  $y'' + 3y' + 2y = 5u(t)$

穩態解  $y_p = \frac{5}{2}u(t), y_p' = 0, y_p'' = 0$

常微分方程 (單變數,  $y$ )

非線性 (有自乘互乘)  
ex.  $y \times y'$

線性

變係數

常係數

齊次 非齊次

插座不亮



60 ↓

单相: 110  $\sqrt{rms}/60Hz$


频率: 电力频率

三相: 3φ 220  $\sqrt{rms}/60Hz$

电压: 电压有效值 振幅  $V_m = \sqrt{2} \times 110$

$$V(t) = \sqrt{2} \times 110 \sin 377t$$

$$V(t) = \sqrt{2} \times 110 \cos 377t$$

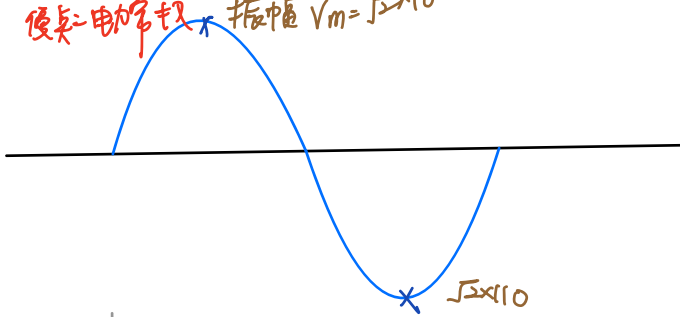

$$f = \frac{1}{T} \quad T = \frac{1}{f} = \frac{1}{60} = 0.0167 \text{ 秒}$$

(秒)

$$\int_{-\pi/2}^{\pi/2} \frac{V_m \cos \theta}{R} d\theta = \frac{V_m^2}{\pi R} \int_{-\pi/2}^{\pi/2} \cos^2 \theta d\theta$$

$\pi$

$$\omega = 2\pi f$$

角频率

$$1 \text{ 周期 } 360^\circ = 2\pi = 6.28 \text{ rad}$$

弧度

$$P(t) =$$

$$\cos(\theta + \theta) = \cos^2 \theta - \sin^2 \theta$$


$$= \cos^2 \theta - [1 - \cos^2 \theta]$$

$$= 2\cos^2 \theta - 1$$

$$\cos^2 \theta = \frac{1 + \cos 2\theta}{2}$$

左同步座標觀察交流

得到直流

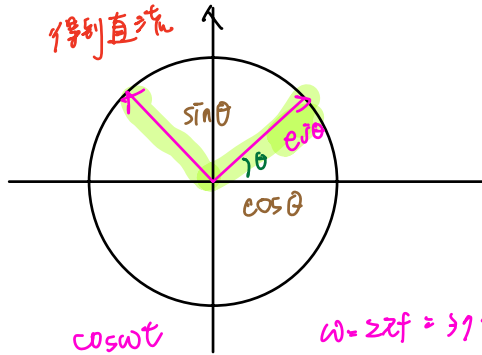

$$\omega = 2\pi f = 377$$

$$V_m e^{j\theta} = [\cos \theta + j \sin \theta] V_m$$

右同步座標視  
不能造

### 三相


$$\pi = 180^\circ$$

$$\frac{2}{3}\pi = 120^\circ$$

$$\left\{ \begin{array}{ll} V_a(t) = 180 \sin 377t & V_a(t) = 180 \cos 377t \\ V_b(t) = 180 \sin(377t - 120^\circ) & V_b(t) = 180 \cos(377t + 120^\circ) \\ V_c(t) = 180 \sin(377t - 240^\circ) & V_c(t) = 180 \cos(377t - 240^\circ) \\ & = 180 \sin(377t + 120^\circ) \\ & = 180 \cos(377t + 240^\circ) \end{array} \right.$$

$$V_m = 180$$
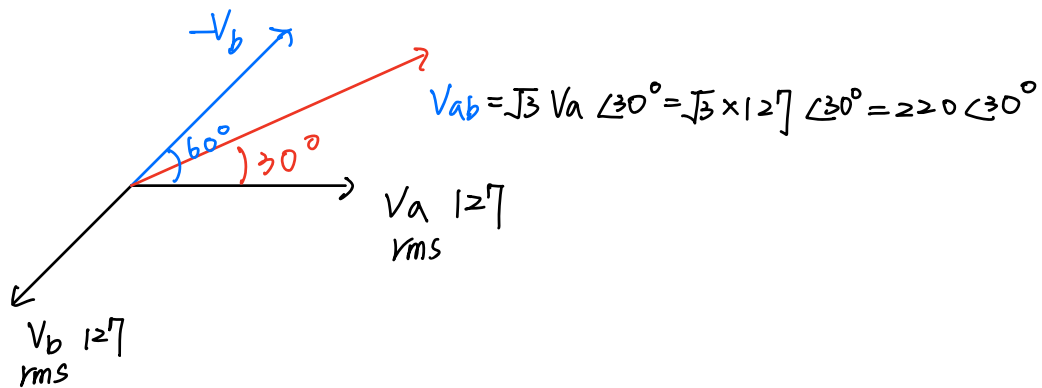
$$\Rightarrow V_{rms} = \frac{V_m}{\sqrt{2}} = 127$$



$$\begin{aligned} V_{ab} &= V_a - V_b \\ &= V_a + (-V_b) \end{aligned}$$

$$V(t) = \frac{1}{C} \int i dt = \frac{1}{C\omega} i \quad \text{領先功因}$$

$$V(t) = i(t) \times R \quad \text{單位功因}$$

$$V(t) = L \frac{di(t)}{dt} \quad \text{落後功因}$$


$$\frac{d}{dt} = s = j\omega$$

$$\frac{d \sin \omega t}{d \omega t} \frac{d \omega t}{dt} = S \sin \omega t$$


$$= \omega \cos \omega t$$

$$= j\omega \sinh \omega t$$

☆ 必考題!
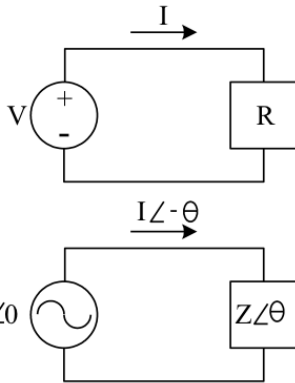
$$P = VI = V^2 / R = I^2 R \quad (1-55)$$
$$v(t) = \sqrt{2} V \cos \omega t \quad (1-56)$$
$$p(t) = v(t)i(t) = 2VI \cos \omega t \cos(\omega t - \theta) \quad (1-58)$$
$$VI \cos \theta \cdot (1 + \cos 2\omega t) + VI \sin \theta \cdot \sin 2\omega t \quad (1-59)$$
$$P \approx VI \cos \theta \quad (1-60)$$
$$S = VI \quad (1-62)$$

$$\sin(A-B) = \sin A \cos B - \cos A \sin B$$
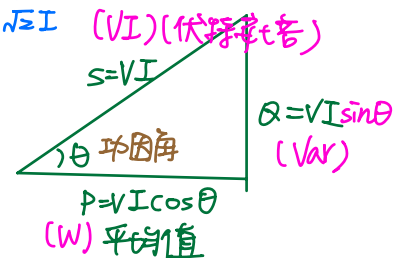
$$V(t) = (j\omega L + R)Z'(t)$$





## 2.1 供應單埠的複數功率

(Complex Power Supplied to a One-Port)

$$v(t) = V_m \cos(\omega t + \theta_v) = \operatorname{Re}(V_m e^{j(\omega t + \theta_v)})$$

$$i(t) = I_m \cos(\omega t + \theta_i) = \operatorname{Re}(I_m e^{j(\omega t + \theta_i)})$$

$$\begin{aligned} p(t) &= v(t) * i(t) = V_m \cos(\omega t + \theta_v) * I_m \cos(\omega t + \theta_i) \\ &= 0.5 * V_m I_m [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)] \end{aligned}$$

Power factor angle:  $\theta = \theta_v - \theta_i$

Power factor =  $\cos\theta$ ; (lagging, leading, unity)

$$\text{Average power} = 0.5 * V_m I_m \cos\theta = V_{\text{rms}} I_{\text{rms}} \cos\theta = \operatorname{Re} VI^*$$

Power triangle  $S = VI^* = P + jQ$ ;

$|S|$  視在功率(VA) apparent power

$S$  複數功率(VA) complex power

$P$  實功(W) real power

$Q$  虛功(無效功率)(Var) reactive power

EX2.1 Inductor  $L$ ,  $Z=j\omega L$ , reactive power  $Q=\omega L|I|^2$

$$i(t)=\sqrt{2}|I|\cos(\omega t+\theta)$$

$$v(t)=Ldi/dt=-\sqrt{2}\omega L|I|\sin(\omega t+\theta)$$

$$\begin{aligned} p(t) &= v(t)*i(t) = -2\omega L|I|^2\sin(\omega t+\theta)\cos(\omega t+\theta) \\ &= -\omega L|I|^2\sin 2(\omega t+\theta) \end{aligned}$$

Average Power  $P=0$ ,

瞬時功不為零 (Instantaneous power is not zero)

但平均值是0

$$S=VI^*=ZII^*=Z|I|^2=j\omega L|I|^2=P+jQ$$

所以  $P=0$ ,  $Q=\text{Im}S=\omega L|I|^2$

練習1: Capacitor  $C$ ,  $Z=1/j\omega C$ , reactive power  $Q=-\omega C|V|^2$

$$v(t)=\sqrt{2}|V|\cos(\omega t+\theta)$$

$$i(t)=Cdv/dt=-\sqrt{2}\omega C|V|\sin(\omega t+\theta)$$

$$\begin{aligned} p(t)=v(t)*i(t) &= -2\omega C|V|^2\sin(\omega t+\theta)\cos(\omega t+\theta) \\ &= -\omega C|V|^2\sin 2(\omega t+\theta) \end{aligned}$$

Average Power  $P=0$ ,

瞬時功不為零(Instantaneous power is not zero)

$$S=VI^*=V(V/Z)^*=|V|^2/(Z)^*=-j\omega C|V|^2=P+jQ$$

$$\text{So } P=0, Q=\text{Im}S=-\omega C|V|^2$$

## 2.2 複數功率守恆

(Conservation of Complex Power)

複數功率守恆( $S_{in} = S_{out}$ ): 數個頻率相同的獨立電源供應的網路，

由各個獨立電源供應的複數功率的總和會等於網路會等於網路上所有分支接收到的複數功率

供電=用電(Power of generators are equal Loads)

## EX2.3 輸入電源並聯電容C

Input voltage with shunt C

$$S_{in} = S_c + S_o$$

$$\begin{aligned} S_c &= VI^* = V(V/Z)^* = VV^*(1/Z)^* = VV^*(Y)^* = |V|^2(SC)^* \\ &= -j\omega C|V|^2 \end{aligned}$$

$$S_o = S_{in} - S_c = S_{in} + j\omega C|V|^2$$

$$P_o = P_{in}$$

$$Q_o = Q_{in} + \omega C|V|^2$$

## EX2.4輸入電源串聯電感L(假設 $|V_2|=|V_1|$ )

Series L between two voltage source

$$S_1 + S_2 = S_L = VI^* = j\omega L |I|^2$$

$$P_1 + P_2 = 0$$

$$Q_1 + Q_2 = Q_L = \omega L |I|^2$$

$$S_1 = V_1 I^*$$

$$S_2 = -V_2 I^*$$

$$\because |V_2| = |V_1| \Rightarrow |S_1| = |S_2| \Rightarrow (P_1)^2 + (Q_1)^2 = (P_2)^2 + (Q_2)^2$$

$$\because |P_2| = |P_1| \Rightarrow |Q_2| = |Q_1| \Rightarrow Q_1 = Q_2 = 0.5\omega L |I|^2$$

$$\text{So } P_1 = -P_2, Q_1 = Q_2 \Rightarrow S_2 = -(S_1)^*$$

## EX2.7三相電源(Three-phase voltages)

以 $n1$ 為基點( $n1$  is basis point)

$$S = V_{an1}I_a^* + V_{bn1}I_b^* + V_{cn1}I_c^* \text{ (三瓦特計法)}$$

以 $b$ 為基點( $b$  is basis point)

$$S = V_{ab}I_a^* + V_{bb}I_b^* + V_{cb}I_c^* = V_{ab}I_a^* + V_{cb}I_c^* \text{ (二瓦特計法)}$$

## 2.3 平衡三相(Balanced Three-Phase) 重要!

### 直流電與交流電的優缺點

Advantages and disadvantages of DC and AC voltages

### 單相交流電與三相交流電的優缺點

Advantages and disadvantages of single-phase voltage and three-phase voltages

### 正序與負序(產生旋轉磁場)，零序


Positive sequence, negative sequence, zero sequence

### 平衡與不平衡電壓和負載(線性與非線性負載)

Balanced and unbalanced voltages and loads

### 中性點電壓與電流(voltage and current of neutral point)

$\Delta$ -Y

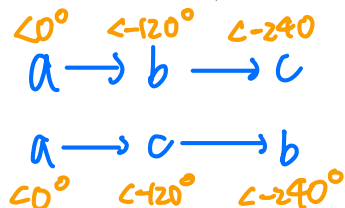



## EX2.8三相電源與負載中性點電壓

Three-phase voltages and neutral point voltage

以 $n$ 為基點( $n$  is basis point)

$$I_a = V_{an}/Z = (V_{an} - V_{nn})/Z = (V_{an} - V_{nn})Y$$


$$I_b = V_{bn}/Z = (V_{bn} - V_{nn})/Z = (V_{bn} - V_{nn})Y$$

$$I_c = V_{cn}/Z = (V_{cn} - V_{nn})/Z = (V_{cn} - V_{nn})Y$$

$$\text{So } I_a + I_b + I_c = (V_{an} + V_{bn} + V_{cn})Y - 3V_{nn}Y = 0$$

$$\text{If } (V_{an} + V_{bn} + V_{cn}) = 0 \Rightarrow V_{nn} = 0$$

EX2.9中性點阻抗不為零時?

$\Delta$ -Y 

阻抗(Impedance)

$$Z_Y = Z_{\Delta}/3$$

$\Delta$ 型負載無法分析, 要變成Y。

EX2.10線對線電壓與相電壓?

Line-to-line voltages and Phase voltages?

## 2.4單相分析(平衡三相)Per Phase Analysis

平衡三相(Balanced three-phase)

**假設**:平衡三相系統；負載與電源是星形連接；電路模型中，相之間無互感存在

**所以**:所有的中性點電位相同；各相是完全去耦合；所有對應的網路變數和平衡電源系統具有相同相序

EX2.11 Balanced three-phase?

## 2.5 平衡三相功率(瞬時功率為常數)

Power of the balanced three-phase is constant

$$S_3 = V_a I_a^* + V_b I_b^* + V_c I_c^*$$

Balanced three-phase and positive sequency 用exponential去消他

$$S_3 = V_a I_a^* + V_a e^{-j2\pi/3} (I_a e^{-j2\pi/3})^* + V_a e^{j2\pi/3} (I_a e^{j2\pi/3})^* = 3 V_a I_a^*$$

Instantaneous Power:  $p_3(t) = p_a(t) + p_b(t) + p_c(t)$

$$p_3(t) = v_a(t) i_a(t) + v_b(t) i_b(t) + v_c(t) i_c(t)$$

$$\begin{aligned} v_a(t) i_a(t) &= V_m \cos(\omega t + \theta_v) I_m \cos(\omega t + \theta_i) \\ &= 0.5 V_m I_m [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)] \end{aligned}$$

$$\begin{aligned} v_b(t) i_b(t) &= V_m \cos(\omega t + \theta_v - 2\pi/3) I_m \cos(\omega t + \theta_i - 2\pi/3) \\ &= 0.5 V_m I_m [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i - 4\pi/3)] \end{aligned}$$

$$\begin{aligned} v_c(t) i_c(t) &= V_m \cos(\omega t + \theta_v + 2\pi/3) I_m \cos(\omega t + \theta_i + 2\pi/3) \\ &= 0.5 V_m I_m [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i + 4\pi/3)] \end{aligned}$$

$$p_3(t) = 3 * 0.5 * V_m I_m [\cos(\theta_v - \theta_i)] = 3 |V| |I| \cos(\theta_v - \theta_i)$$

## 2.6 複數功率傳輸(短程) Complex power Transmission

加電容, 加電感

100 km ↓

短程輸電線，用串聯的RL電路來表示電線  $Z=R+j\omega L$

$$V_1=|V_1|e^{j\theta_1}, V_2=|V_2|e^{j\theta_2}, Z=|Z|e^{j\angle Z}, \theta_{12}=\theta_1-\theta_2$$

$$S_{12}=V_1 I_1^*=V_1[(V_1-V_2)/Z]^*=|V_1|^2/(Z)^*-V_1 V_2^*/(Z)^*$$

$$=|V_1|^2 e^{j\angle Z}/|Z|-|V_1||V_2| e^{j\angle Z} e^{j\theta_{12}}/|Z|$$

$$S_{21}=|V_2|^2 e^{j\angle Z}/|Z|-|V_1||V_2| e^{j\angle Z} e^{-j\theta_{12}}/|Z|$$

$$\text{Assume } R=0, Z=jX \Rightarrow \angle Z=90^\circ, e^{j\angle Z}=j$$

$$\text{So } P_{12}=-P_{21}=(|V_1||V_2|/X)\sin\theta_{12}$$


$$Q_{12}=|V_1|^2/X - (|V_1||V_2|/X)\cos\theta_{12}$$

$$Q_{21}=|V_2|^2/X - (|V_1||V_2|/X)\cos\theta_{12}$$

EX2.12 兩個發電機失去同步? Two generators without synchronous?


$$P_{12}=-P_{21}=(|V_1||V_2|/X)\sin[(\omega_1-\omega_2)t+\theta_{12}]$$

電力系統 ① 只有一部發電機 (少數)

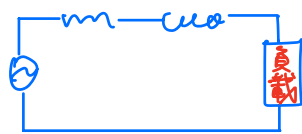

② 兩部發電機

③ 多個發電機

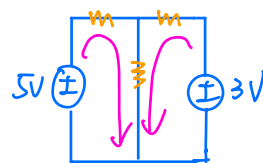

EX2.13(短程 short distance)  $Z=1 \angle 85^\circ$  ,  $\theta_{12}=10^\circ$

$$(a) |V_1|=|V_2|=1$$

$$\begin{aligned} S_{12} &= V_1 I_1^* = V_1 [(V_1 - V_2)/Z]^* = |V_1|^2/(Z)^* - V_1 V_2^*/(Z)^* \\ &= |V_1|^2 e^{j\angle Z} / |Z| - |V_1||V_2| e^{j\angle Z} e^{j\theta_{12}} / |Z| \end{aligned}$$

$$S_{12} = 1 \angle 85^\circ - 1 \angle 95^\circ$$

$$S_{21} = |V_2|^2 e^{j\angle Z} / |Z| - |V_1||V_2| e^{j\angle Z} e^{-j\theta_{12}} / |Z|$$

$$S_{21} = 1 \angle 85^\circ - 1 \angle 75^\circ$$

$$P_{12} = -P_{21} = 0.1743$$

$$Q_{12} = 0$$

$$Q_{21} = 0.0303$$

$$(b) |V_1|=1.1 \text{ , } |V_2|=0.9 \text{ , } Z=1 \angle 85^\circ \text{ , } \theta_{12}=10^\circ$$

EX2.14 SG1:  $V_1 = 1 \angle 0^\circ$  ,  $SD_1 = 1$  ,  $jQ_{G2} : V_2 = ?$  ,  $SD_2 = 1$  ,  $Z = j0.5$

(a) Find  $Q_{G2}$  for  $|V_2| = 1$  (b) and  $\angle V_2$  ? (c) If  $Q_{G2} = 0$ , could be supplied load  $SD_2$  ? (d) and  $\angle V_2$  ?

$\therefore SD_2 = 1$  real , and  $jQ_{G2}$  imaginary number , So  $P_{12} = -P_{21} = 1$

So  $P_{12} = -P_{21} = (|V_1||V_2|/X)\sin\theta_{12} = 2\sin\theta_{12} = 1$

So  $\theta_{12} = 30^\circ$  , and  $\angle V_2 = -30^\circ$

$Q_{G2} = Q_{21} = |V_2|^2/X - (|V_1||V_2|/X)\cos\theta_{12} = 2 - 2\cos 30^\circ = 0.268$

(c) and (d)

If  $Q_{G2} = 0$ ,  $-S_{21} = SD_2 = 1$

$S_{21} = |V_2|^2 e^{j\angle Z} / |Z| - |V_1||V_2| e^{j\angle Z} e^{-j\theta_{12}} / |Z| =$

Find  $2|V_2|^2 = 1$ ,  $\theta_{12} = 45^\circ \Rightarrow V_2 = 0.707 \angle -45^\circ$


(c) and (d)

If  $Q_{G2} = 0$ , so  $Q_{G2} = Q_{21} = |V_2|^2/X - (|V_1||V_2|/X)\cos\theta_{12} = 0$

so  $|V_2| = |V_1|\cos\theta_{12} = \cos\theta_{12}$

If  $P_{12} = -P_{21} = (|V_1||V_2|/X)\sin\theta_{12} = 2|V_2|\sin\theta_{12} = 1$

so  $\theta_{12} = 45^\circ$ ,  $|V_2| = 0.707$

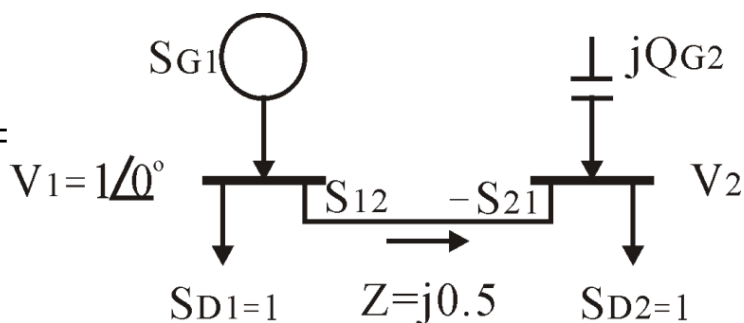



## 2.7 複數功率傳輸(輻射線路)

### Complex Power Transmission: Radial Line

較遠的一端有複數功率負載，沒有發電機或電容器組來維持電壓，求遠端電壓受負載變化的影響？

$$S_D = V_2 I^* = |V_2| |I| e^{j\psi}$$

$$= |V_2| |I| (\cos\psi + j\sin\psi) = P_D (1 + j\beta)$$

$$P_D = P_{12} = -P_{21} = (|V_1| |V_2| / X) \sin\theta_{12}$$

$$Q_D = -Q_{21} = -|V_2|^2 / X + (|V_1| |V_2| / X) \cos\theta_{12}$$

## 2.8結論與習題(Summary)

瞬時功率(Instantaneous Power)

複數功率(Complex Power)

有效功率(Real Power)

無效功率(Reactive Power)

相量(Phasor)

平衡三相(Balanced Three-Phase)

單相分析(Per Phase Analysis)

