

# Power System Analysis

供電=用電

Arthur R. Bergen

授課：侯中權 博士

(Prof. Chung-Chuan Hou)

## 2. 基本原理(Basic Principles)

2.0 簡介(Introduction)

2.1 供應單埠的複數功率(Complex Power Supplied to a One-Port)

2.2 複數功率守恆(Conservation of Complex Power)

2.3 平衡三相(Balanced Three-Phase)

2.4 單相分析(Per Phase Analysis)

2.5 平衡三相功率(Balanced Three-Phase Power)

2.6 複數功率傳輸(短程)(Complex Power Transmission)

2.7 複數功率傳輸(輻射線路) (Complex Power Transmission: Radial Line)

2.8 結論與習題(Summary)

## 2.0 簡介(Introduction)

1 直流電:被動元件(R,L,C);  $V=IR$ ,  $V=Ldi/dt$ ,  $I=Cdv/dt$

功率  $P=VI=V^2/R=I^2R$ ; 功  $J=P*t$

2 Kirchhoff's current law (KCL): sum of currents entering a node (or a closed boundary) is zero.

3 Kirchhoff's voltage law (KVL): sum of all voltages around a closed path (or loop) is zero.

4 穩態、暫態、動態 (steady state, transient state, dynamic state)

5 交流電:單相與三相;相量(phasor)

6 交流電:被動元件(R,L,C);  $v=iR$ ,  $v=Ldi/dt$ ,  $i=Cdv/dt$

功率  $P=V_{rms}I_{rms}=V_{rms}^2/R=I_{rms}^2R$ ; 功  $J=P*t$

7 符號:  $V_{BE}$ (總瞬間值) =  $V_{BE}$ (直流值) +  $v_{be}$ (交流瞬間值)

$V_{be}$ (相量值)

## 2.1 供應單埠的複數功率

### (Complex Power Supplied to a One-Port)

$$v(t) = V_m \cos(\omega t + \theta_v) = \operatorname{Re}(V_m e^{j(\omega t + \theta_v)})$$

$$i(t) = I_m \cos(\omega t + \theta_i) = \operatorname{Re}(I_m e^{j(\omega t + \theta_i)})$$

$$\begin{aligned} p(t) &= v(t) * i(t) = V_m \cos(\omega t + \theta_v) * I_m \cos(\omega t + \theta_i) \\ &= 0.5 * V_m I_m [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)] \end{aligned}$$

Power factor angle:  $\theta = \theta_v - \theta_i$

Power factor =  $\cos\theta$ ; (lagging, leading, unity)

$$\text{Average power} = 0.5 * V_m I_m \cos\theta = V_{\text{rms}} I_{\text{rms}} \cos\theta = \operatorname{Re} VI^*$$

Power triangle  $S = VI^* = P + jQ$ ;

$|S|$  視在功率 (VA) apparent power

$S$  複數功率 (VA) complex power

$P$  實功 (W) real power

$Q$  虛功 (無效功率) (Var) reactive power

EX2.1 Inductor  $L$ ,  $Z=j\omega L$ , reactive power  $Q=\omega L|I|^2$

$$i(t)=\sqrt{2}|I|\cos(\omega t+\theta)$$

$$v(t)=Ldi/dt=-\sqrt{2}\omega L|I|\sin(\omega t+\theta)$$

$$\begin{aligned} p(t)=v(t)*i(t) &= -2\omega L|I|^2\sin(\omega t+\theta)\cos(\omega t+\theta) \\ &= -\omega L|I|^2\sin 2(\omega t+\theta) \end{aligned}$$

Average Power  $P=0$ ,

瞬時功不為零 (Instantaneous power is not zero)

$$S=VI^*=ZII^*=Z|I|^2=j\omega L|I|^2=P+jQ$$

所以  $P=0$ ,  $Q=\text{Im}S=\omega L|I|^2$

練習 1: Capacitor  $C$ ,  $Z=1/j\omega C$ , reactive power  $Q=-\omega C|V|^2$

$$v(t)=\sqrt{2}|V|\cos(\omega t+\theta)$$

$$i(t)=Cdv/dt=-\sqrt{2}\omega C|V|\sin(\omega t+\theta)$$

$$\begin{aligned} p(t)=v(t)*i(t) &= -2\omega C|V|^2\sin(\omega t+\theta)\cos(\omega t+\theta) \\ &= -\omega C|V|^2\sin 2(\omega t+\theta) \end{aligned}$$

Average Power  $P=0$ ,

瞬時功不為零 (Instantaneous power is not zero)

$$S=VI^*=V(V/Z)^*=|V|^2/(Z)^*=-j\omega C|V|^2=P+jQ$$

$$\text{So } P=0, Q=\text{Im}S=-\omega C|V|^2$$

## 2.2 複數功率守恆 (Conservation of Complex Power)

複數功率守恆( $S_{in} = S_{out}$ ): 數個頻率相同的獨立電源供應的網路，

由各個獨立電源供應的複數功率的總和會等於網路  
會等於網路上所有分支接收到的複數功率

供電=用電(Power of generators are equal Loads)

## EX2.3 輸入電源並聯電容C

### Input voltage with shunt C

$$S_{in} = S_c + S_o$$

$$\begin{aligned} S_c &= VI^* = V(V/Z)^* = VV^*(1/Z)^* = VV^*(Y)^* = |V|^2(SC)^* \\ &= -j\omega C|V|^2 \end{aligned}$$

$$S_o = S_{in} - S_c = S_{in} + j\omega C|V|^2$$

$$P_o = P_{in}$$

$$Q_o = Q_{in} + \omega C|V|^2$$



## EX2.4 輸入電源串聯電感L(假設 $|V_2|=|V_1|$ )

### Series L between two voltage source

$$S_1 + S_2 = S_L = VI^* = j\omega L |I|^2$$

$$P_1 + P_2 = 0$$

$$Q_1 + Q_2 = Q_L = \omega L |I|^2$$

$$S_1 = V_1 I^*$$

$$S_2 = -V_2 I^*$$

$$\because |V_2| = |V_1| \Rightarrow |S_1| = |S_2| \Rightarrow (P_1)^2 + (Q_1)^2 = (P_2)^2 + (Q_2)^2$$

$$\because |P_2| = |P_1| \Rightarrow |Q_2| = |Q_1| \Rightarrow Q_1 = Q_2 = 0.5\omega L |I|^2$$

$$\text{So } P_1 = -P_2, \quad Q_1 = Q_2 \Rightarrow S_2 = -(S_1)^*$$

## EX2.7 三相電源(Three-phase voltages)

以n1為基點(n1 is basis point)

$$S = V_{an1} I_a^* + V_{bn1} I_b^* + V_{cn1} I_c^* \text{ (三瓦特計法)}$$

以b為基點(b is basis point)

$$S = V_{ab} I_a^* + V_{bb} I_b^* + V_{cb} I_c^* = V_{ab} I_a^* + V_{cb} I_c^* \text{ (二瓦特計法)}$$

## 2.3 平衡三相(Balanced Three-Phase)

直流電與交流電的優缺點

Advantages and disadvantages of DC and AC voltages

單相交流電與三相交流電的優缺點

Advantages and disadvantages of single-phase voltage and three-phase voltages

正序與負序(產生旋轉磁場)，零序

Positive sequence, negative sequence, zero sequence

平衡與不平衡電壓和負載(線性與非線性負載)

Balanced and unbalanced voltages and loads

中性點電壓與電流(voltage and current of neutral point)

$\Delta$ -Y

## EX2.8 三相電源與負載中性點電壓

### Three-phase voltages and neutral point voltage

以n1為基點(n1 is basis point)

$$I_a = V_{an1}/Z = (V_{an} - V_{n1n})/Z = (V_{an} - V_{n1n})Y$$

$$I_b = V_{bn1}/Z = (V_{bn} - V_{n1n})/Z = (V_{bn} - V_{n1n})Y$$

$$I_c = V_{cn1}/Z = (V_{cn} - V_{n1n})/Z = (V_{cn} - V_{n1n})Y$$

$$\text{So } I_a + I_b + I_c = (V_{an} + V_{bn} + V_{cn})Y - 3V_{n1n}Y = 0$$

$$\text{If } (V_{an} + V_{bn} + V_{cn}) = 0 \Rightarrow V_{n1n} = 0$$

EX2.9 中性點阻抗不為零時?

$\Delta$ -Y

阻抗(Impedance)

$$Z_Y = Z_{\Delta} / 3$$

EX2.10 線對線電壓與相電壓？

Line-to-line voltages and Phase voltages?

## 2.4單相分析(平衡三相)Per Phase Analysis

平衡三相(Balanced three-phase)

**假設:**平衡三相系統；負載與電源是星形連接；電路模型中，相之間無互感存在

**所以:**所有的中性點電位相同；各相是完全去耦合；所有對應的網路變數和平衡電源系統具有相同相序

EX2.11 Balanced three-phase?

## 2.5 平衡三相功率(瞬時功率為常數)

Power of the balanced three-phase is constant

$$S_3 = V_a I_a^* + V_b I_b^* + V_c I_c^*$$

Balanced three-phase and positive sequency

$$S_3 = V_a I_a^* + V_a e^{-j2\pi/3} (I_a e^{-j2\pi/3})^* + V_a e^{j2\pi/3} (I_a e^{j2\pi/3})^* = 3 V_a I_a^*$$

Instantaneous Power:  $p_3(t) = p_a(t) + p_b(t) + p_c(t)$

$$p_3(t) = v_a(t) i_a(t) + v_b(t) i_b(t) + v_c(t) i_c(t)$$

$$\begin{aligned} v_a(t) i_a(t) &= V_m \cos(\omega t + \theta_v) * I_m \cos(\omega t + \theta_i) \\ &= 0.5 * V_m I_m [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)] \end{aligned}$$

$$\begin{aligned} v_b(t) i_b(t) &= V_m \cos(\omega t + \theta_v - 2\pi/3) * I_m \cos(\omega t + \theta_i - 2\pi/3) \\ &= 0.5 * V_m I_m [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i - 4\pi/3)] \end{aligned}$$

$$\begin{aligned} v_c(t) i_c(t) &= V_m \cos(\omega t + \theta_v + 2\pi/3) * I_m \cos(\omega t + \theta_i + 2\pi/3) \\ &= 0.5 * V_m I_m [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i + 4\pi/3)] \end{aligned}$$

$$p_3(t) = 3 * 0.5 * V_m I_m [\cos(\theta_v - \theta_i)] = 3 |V| |I| \cos(\theta_v - \theta_i)$$

## 2.6複數功率傳輸(短程)Complex power Transmission

短程輸電線，用串聯的RL電路來表示電線 $Z=R+j\omega L$

$$V_1=|V_1|e^{j\theta_1}, V_2=|V_2|e^{j\theta_2}, Z=|Z|e^{j\angle Z}, \theta_{12}=\theta_1-\theta_2$$

$$\begin{aligned} S_{12}=V_1 I_1^* &= V_1 [(V_1-V_2)/Z]^* = |V_1|^2/(Z)^* - V_1 V_2^*/(Z)^* \\ &= |V_1|^2 e^{j\angle Z}/|Z| - |V_1||V_2| e^{j\angle Z} e^{j\theta_{12}}/|Z| \end{aligned}$$

$$S_{21}=|V_2|^2 e^{j\angle Z}/|Z| - |V_1||V_2| e^{j\angle Z} e^{-j\theta_{12}}/|Z|$$

$$\text{Assume } R=0, Z=jX \Rightarrow \angle Z=90^\circ, e^{j\angle Z}=j$$

$$\text{So } P_{12} = -P_{21} = (|V_1||V_2|/X) \sin \theta_{12}$$

$$Q_{12} = |V_1|^2/X - (|V_1||V_2|/X) \cos \theta_{12}$$

$$Q_{21} = |V_2|^2/X - (|V_1||V_2|/X) \cos \theta_{12}$$

EX2.12兩個發電機失去同步? Two generators without synchronous?

$$P_{12} = -P_{21} = (|V_1||V_2|/X) \sin[(\omega_1 - \omega_2)t + \theta_{12}]$$



EX2.13(短程 short distance)  $Z=1\angle 85^\circ$  ,  $\theta_{12}=10^\circ$

$$(a)|V_1|=|V_2|=1$$

$$S_{12}=V_1 I_1^*=V_1[(V_1-V_2)/Z]^*=|V_1|^2/(Z)^*-V_1 V_2^*/(Z)^* \\ =|V_1|^2 e^{j\angle Z}/|Z|-|V_1||V_2| e^{j\angle Z} e^{j\theta_{12}}/|Z|$$

$$S_{12}=1\angle 85^\circ -1\angle 95^\circ$$

$$S_{21}=|V_2|^2 e^{j\angle Z}/|Z|-|V_1||V_2| e^{j\angle Z} e^{-j\theta_{12}}/|Z|$$

$$S_{21}=1\angle 85^\circ -1\angle 75^\circ$$

$$P_{12}=-P_{21}=0.1743$$

$$Q_{12}=0$$

$$Q_{21}=0.0303$$

$$(b)|V_1|=1.1 \text{ , } |V_2|=0.9 \text{ , } Z=1\angle 85^\circ \text{ , } \theta_{12}=10^\circ$$

EX2.14  $S_{G1}:V_1=1\angle 0^\circ$  ,  $S_{D1}=1$  ,  $jQ_{G2}:V_2=?$  ,  $S_{D2}=1$  ,  $Z=j0.5$

(a) Find  $Q_{G2}$  for  $|V_2|=1$  (b) and  $\angle V_2$  ? (c) If  $Q_{G2}=0$ , could be supplied load  $S_{D2}$  ? (d) and  $\angle V_2$  ?

$\because S_{D2}=1$  real , and  $jQ_{G2}$  imaginary number , So  $P_{12} = -P_{21}=1$

So  $P_{12} = -P_{21} = (|V_1||V_2|/X)\sin\theta_{12} = 2\sin\theta_{12} = 1$

So  $\theta_{12}=30^\circ$  , and  $\angle V_2 = -30^\circ$

$Q_{G2} = Q_{21} = |V_2|^2/X - (|V_1||V_2|/X)\cos\theta_{12} = 2 - 2\cos 30^\circ = 0.268$

**(c) and (d)**

If  $Q_{G2}=0$ ,  $-S_{21} = S_{D2}=1$

$S_{21} = |V_2|^2 e^{j\angle Z} / |Z| - |V_1||V_2| e^{j\angle Z} e^{-j\theta_{12}} / |Z| = -1$

Find  $2|V_2|^2=1, \theta_{12}=45^\circ \Rightarrow V_2=0.707\angle -45^\circ$


**(c) and (d)**

If  $Q_{G2}=0$ , so  $Q_{G2} = Q_{21} = |V_2|^2/X - (|V_1||V_2|/X)\cos\theta_{12} = 0$

so  $|V_2| = |V_1|\cos\theta_{12} = \cos\theta_{12}$

If  $P_{12} = -P_{21} = (|V_1||V_2|/X)\sin\theta_{12} = 2|V_2|\sin\theta_{12} = 1$

so  $\theta_{12}=45^\circ$  ,  $|V_2|=0.707$

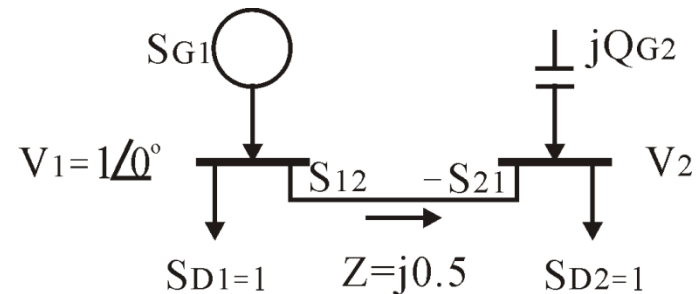

## 2.7 複數功率傳輸(輻射線路)

### Complex Power Transmission: Radial Line

較遠的一端有複數功率負載，沒有發電機或電容器組來維持電壓，求遠端電壓受負載變化的影響？

$$S_D = V_2 I^* = |V_2| |I| e^{j\psi}$$

$$= |V_2| |I| (\cos\psi + j\sin\psi) = P_D (1 + j\beta)$$

$$P_D = P_{12} = -P_{21} = (|V_1| |V_2| / X) \sin\theta_{12}$$

$$Q_D = -Q_{21} = -|V_2|^2 / X + (|V_1| |V_2| / X) \cos\theta_{12}$$

## 2.8結論與習題(Summary)

瞬時功率(Instantaneous Power)

複數功率(Complex Power)

有效功率(Real Power)

無效功率(Reactive Power)

相量(Phasor)

平衡三相(Balanced Three-Phase)

單相分析(Per Phase Analysis)