
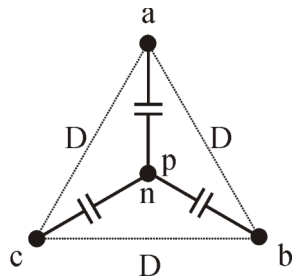


2022/05/31 電力工程導論 姓名_____ 學號_____

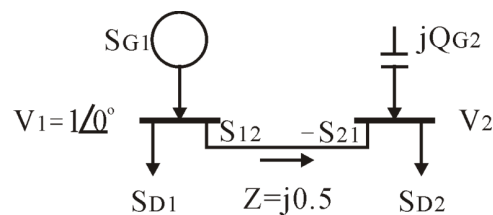
1. (20) Assume that 1. conductors are equally spaced, D , and have equal radii r . 2. $q_a + q_b + q_c = 0$ ($c_a = c_b = c_c = c$, $v_a + v_b + v_c = 0$) 3. $i_a + i_b + i_c = 0$. Find (a) $c = ?$ (b) $\lambda_a = ?$



2. (20) A 60-Hz 138-kV 3 Φ transmission line is 225 mile long. The distributed line parameters are $r = 0.169 \Omega/\text{mile}$, $l = 2.093 \text{ mH}/\text{mile}$, $c = 0.01427 \mu\text{F}/\text{mile}$, $g = 0$. The transmission line delivers 40 Mwat 132 kV with 95% power factor lagging. (a) Find the sending-end voltage and current. (b) Find the transmission line efficiency.
3. (20) $V_1 = 1 \angle 0^\circ$, $jQ_{G2} = j1.0$, $Z_L = j0.5$, $S_{D2} = P_{D2} + j1.0$. Find S_1 and V_2 . We consider the solution as a function of P_{D2} for $P_{D2} \geq 0$. (a) If $P_{D2} > 1 \Rightarrow V_2 = ?$ (b) If $P_{D2} = 1 \Rightarrow V_2 = ?$ (c) If $P_{D2} = 0.5 \Rightarrow V_2 = ?$



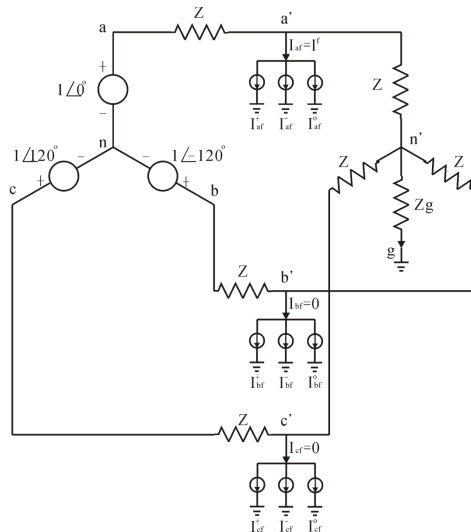4. (20) Fault current: $I^f = [I_{af} \ I_{bf} \ I_{cf}] = [I^f \ 0 \ 0]$. Find the symmetrical components of single line-to-ground faults currents.



5. (20) $v_a = 180 \cos \omega t$, $v_b = 180 \cos (\omega t - 120^\circ)$, $v_c = 180 \cos (\omega t + 120^\circ)$ (a) Find abc Reference Frame to Stationary Reference Frame (b) Stationary Reference Frame to Synchronous Reference Frame